## Embedded Computer Design

(DISEÑO DE COMPUTADORES EMPOTRADOS)

Course 2017/18

# Introduction to Basics Components


#### Professors:

- Arturo Morgado Estévez
- Mirian Cifredo Chacón


Computer Engineering Degree

- Shopping for electronics components
  - http://es.farnell.com/
  - <a href="http://es.rs-online.com">http://es.rs-online.com</a>
  - http://www.digikey.es/
- Robotics shops in Spain
  - http://www.cooking-hacks.com/
  - http://www.bricogeek.com/shop/

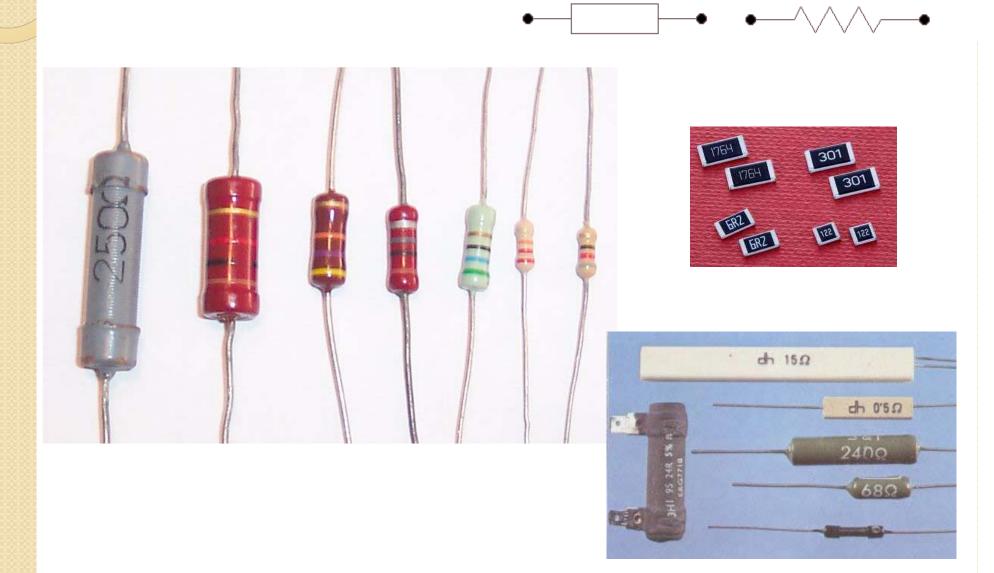
- Basics Components. Resistor.
  - Termination style. Axial and SMD.



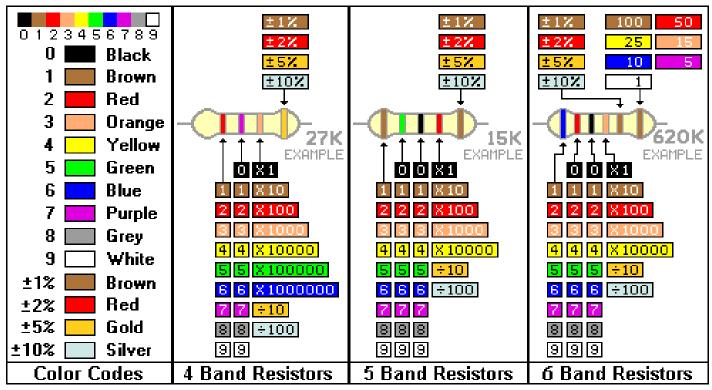- Basics Components. Resistor.
  - Values.



#### **SMD Resistors Cheat Sheet**

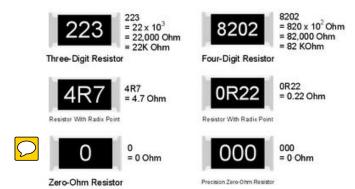


- Basics Components. Resistor.
  - Series and parallel resistors.


$$R = \frac{V}{I}$$

$$R_1 = R_1 + R_2 + R_3 + .... R_n$$


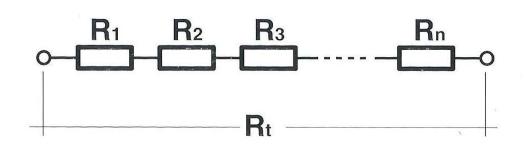
$$R_{t} = \frac{1}{\frac{1}{B_{1} + B_{2} + B_{3} + B_{3}}}$$



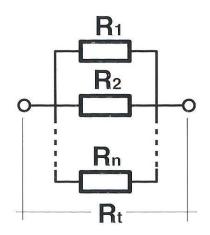

SERIE -WM-WM-
$$R_{1} = R_{1} + R_{2}$$

$$PARALELO - R_{1} = \frac{1}{R_{1}} + \frac{1}{R_{2}}$$

$$R_{2}$$

- Basics Components. Resistor. Preferred values.
  - Resistors kits I/4W.
    - Values:
      - 0Ω, 1.5Ω, 4.7Ω, 10Ω, 47Ω
      - 110Ω, 220Ω, 330Ω, 470Ω, 680Ω
      - IkΩ, 2.2kΩ, 3.3kΩ, 4.7kΩ, 10kΩ
      - 22kΩ, 47kΩ, 100kΩ, 330kΩ, 1MΩ.



E12	E24	E48	E12	E24	E48
100	100	100	330	330	316
		105			332
	110	110		360	348
		115			365
120	120	121	390	390	383
		127			402
	130	133		430	422
		140			442
150	150	147	470	470	464
		154			487
	160	162		510	511
		169			536
180	180	178	560	560	562
		187			590
	200	196		620	619
e fan en earle		205			649
220	220	215	680	680	681
		226			715
	240	237		750	750
		249			787
270	270	261	820	820	825
		274			866
	300	287		910	909
		301			953

- Basics Components. Potentiometers.
- Lineal

**Potentiometers** 




**Potentiometers** 








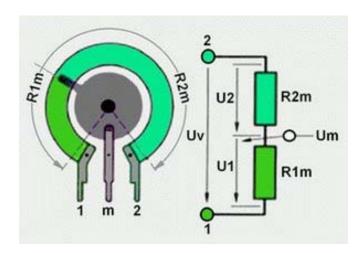








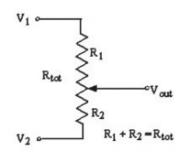

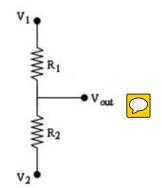

- Basics Components. Potentiometers.
  - Potentiometer I0K LIN.

Track Resistance: 10kohm

Track Taper: Lineal

Shaft Diameter: 6.35mm

Shaft Length - Metric: 51mm


Resistance Tolerance: ± 20%

Nominal Power: 400mW

http://www.tycoelectronics.com/commerce/DocumentDelivery/DDEController?Action=srchrtrv&DocNm=1773115&DocType=Data+Sheet&DocLang=English




Basics Components. Capacitor.

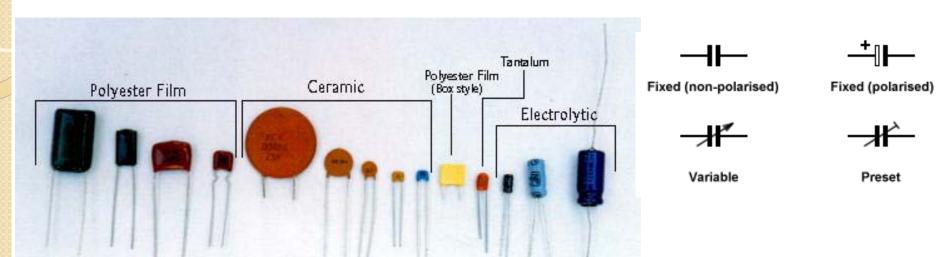






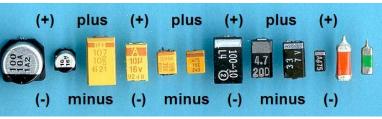

Basics Components. Capacitor. Values.

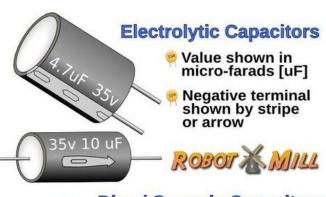


/ Cerami	c Capacitors
Value sł pico-far	nown in ads [pF]
(1 pF =	0.000001 uF)
Non-pol (no + / -	ar terminals)
	t is multiplier = 150000 pF
0 = x1 1 = x10	4 = x10000 5 = x100000
	<ul> <li>Value st pico-far (1 pF =</li> <li>Non-pol (no + / -</li> <li>3rd digir ex: 154</li> <li>0 = x1</li> </ul>

2 = x100


 $3 = x1000 \mid 9 = x.1$ 


8 = x.01

Type	Pic	Cap Range	ESR	Leakage	Voltage Rating	Temp Range	Gen Notes
Ceramic		pF - μF	low	med	high	-55° to +125°C	Multipurpose Cheap
Mica (silver mica)	**	pF - nF	low 0.01-0.1Ω	low	high	-55° to +125°C	For RF filters Expensive Very stable
Plastic Film (polyethylene polystyrene)	WIMA 0.047 UF 1000.	few μFs	med	med	high	varies	For low freq Cheap
Tantalum		μFs	high 0.5-5.0Ω	low	lowest	-55° to +125°C	Expensive Nonlinear (bad for audio)
oscon	9	μFs	low 0.01-0.5Ω	low	low	-55° to +105°C	Best quality Highest price
Aluminum Electrolytic		high μFs	high 0.05-2.0Ω	med	low	-40° to +85°C	For low-med frequencies Cheap Hold charge for long time – not for production test

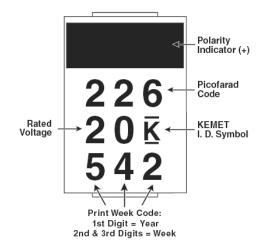

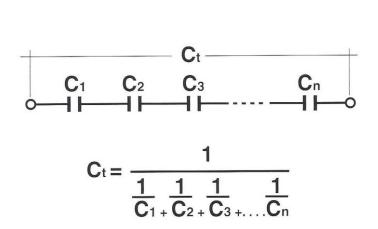• Basics Components. Series and parallel Capacitor.




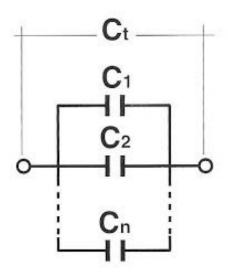



$$C_t = C_1 + C_2 + C_3 + ... \cdot C_n$$

Basics Components. Diode.




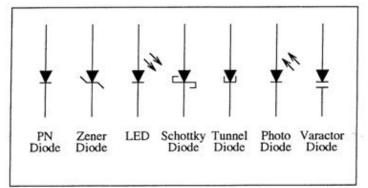


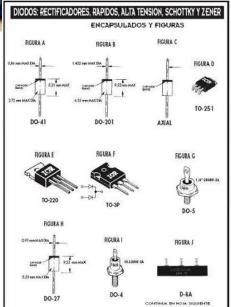


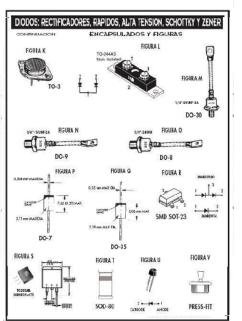


• Basics Components. Diode.

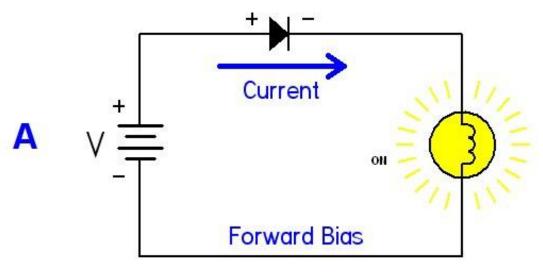

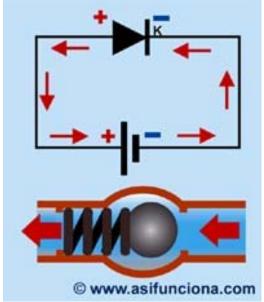

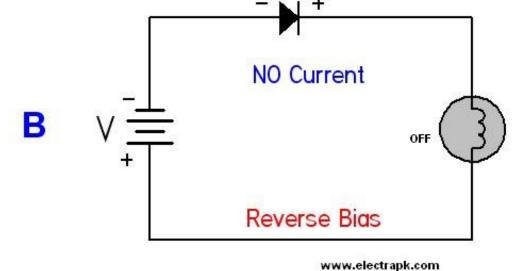

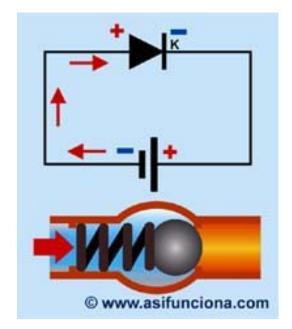

- Basics Components. Diode.
  - General purpose IN4148 @ 200mA
  - http://www.fairchildsemi.com/ds/1N/1N4148.pdf

Basics Components. LED. Types.



- Basics Components. LED.
  - Ultraviolet LED 5mm 395-400nm
  - Features:
    - T1 3/4 5mm clear lens
    - 395-400nm


 $\bigcirc$ 


- 100-180mcd
- 3-3.6V forward drop




 http://www.sparkfun.com/datasheets/Components/LED/YSL-R547P4C-E3.pdf

Basics Components. Voltage Regulator.

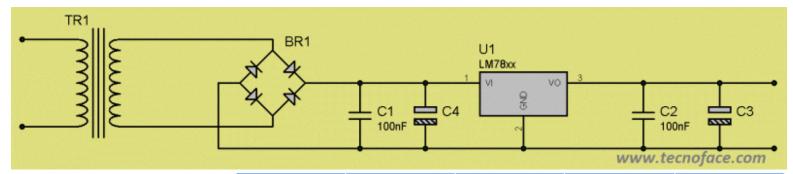


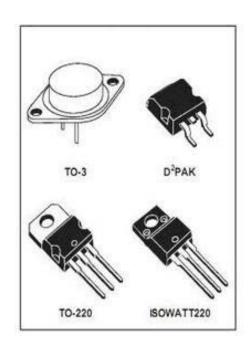

Tensión de salida	U1	C3	C4	TR-1
5v	LM7805	100uF - 16v	1000uF - 16v	220v a 9v
6v	LM7806	100uF - 16v	1000uF - 16v	220v a 9v
8v	LM7808	100uF - 16v	1000uF - 25v	220v a 12v
9v	LM7809	100uF - 16v	1000uF - 25v	220v a 12v
12v	LM7812	100uF - 25v	1000uF - 35v	220v a 15v
15v	LM7815	100uF - 25v	1000uF - 35v	220v a 18v
24v	LM7824	100uF - 35v	1000uF - 40v	220v a 24v

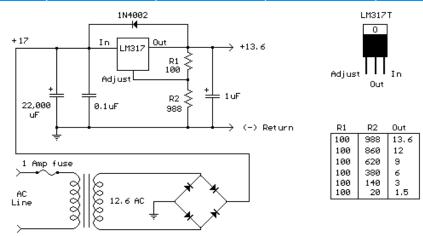


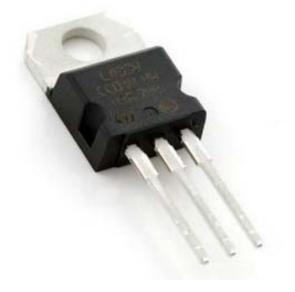
- Basics Components. Voltage Regulator.
  - LD1117V33,.3.3V Regulator
    - 800mA Max
    - TO-220




http://www.sparkfun.com/datasheets/Components/LD1117V33.pdf

Basics Components. Transistors. Types.

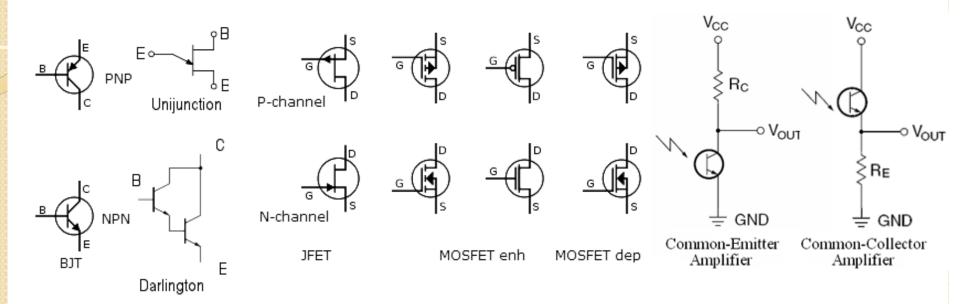

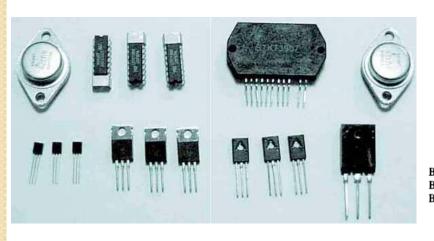

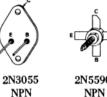












PC100 NPN

2N6099 PC110 NPN BDX53 NPN

BDX54 NPN BD135 NPN BD139 NPN

 BD131 NPN BD137 NPN MC140 NPN BD132 NPN BD138 PNP MC150 PNP








BC547 NPN BC548 NPN BC549 NPN


BSX20 NPN 2N3866 NPN 2N3924 NPN

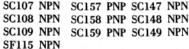


SC108 NPN SC158 PNP SC148 NPN SC109 NPN SC159 PNP SC149 NPN

AC126 PNP AC127 NPN AC128 PNP

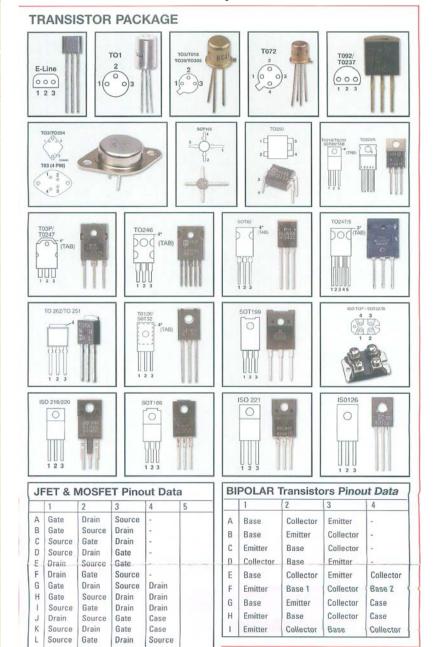
Basics Components. Transistors. Packaging.




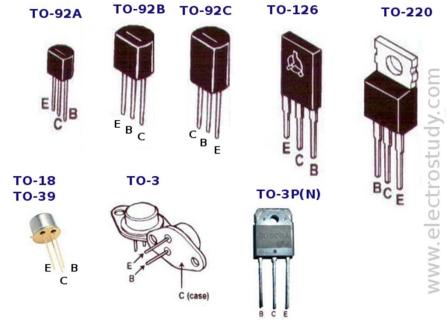

FIGURAS	DENOMINACIÓN	IMAGEN
28-30 mm	SOT-23	1
1.8.22 ms	SOT-223	1
53-57m	SOT-323/SC-70	
4.4-46 m 2.4-26 m	SOT-89	

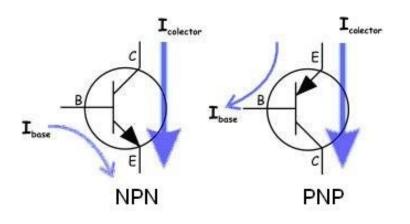• Basics Components. Transistors. Simplified operation.



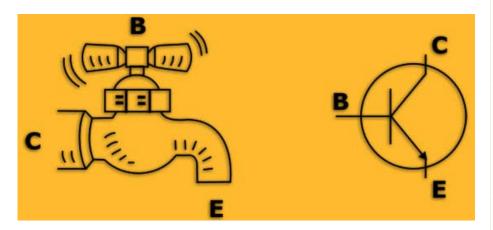

- Basics Components. Transistors.
  - Transistor NPN 2N3904
    - Transistor NPN.
    - <a href="http://www.sparkfun.com/datasheets/Components/2N3904.pdf">http://www.sparkfun.com/datasheets/Components/2N3904.pdf</a>



## Embedded Computer Design

(DISEÑO DE COMPUTADORES EMPOTRADOS)

Course 2017/18

# Introduction to Basics Components

#### Professors:

- Arturo Morgado Estévez
- Mirian Cifredo Chacón

Computer Engineering Degree